

**Class Test 1**  
**ICE 1205: Circuit Theory and Analysis**

Time: 30 minutes

Marks: 10

- Q.1** Define power and energy. What is the output in horsepower of a motor with an efficiency of 80% and an input current of 8 A at 120 V? 4
- Q.2** For the series circuit in Fig.1 6

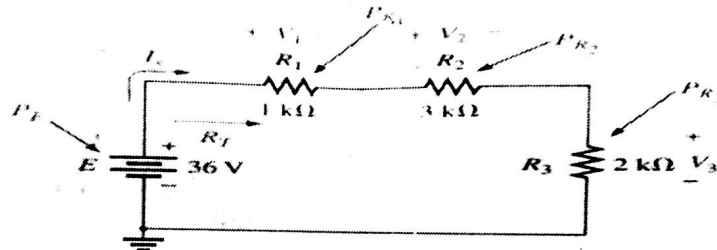


Fig.1


- Determine the total resistance  $R_T$ .
- Calculate the current  $I_s$ .
- Determine the voltage across each resistor.
- Find the power supplied by the battery.
- Determine the power dissipated by each resistor.
- Comment on whether the total power supplied equals the total power dissipated.

**Class Test 2**  
**ICE 1205: Circuit Theory and Analysis**

**Time: 30 minutes**

**Marks: 10**

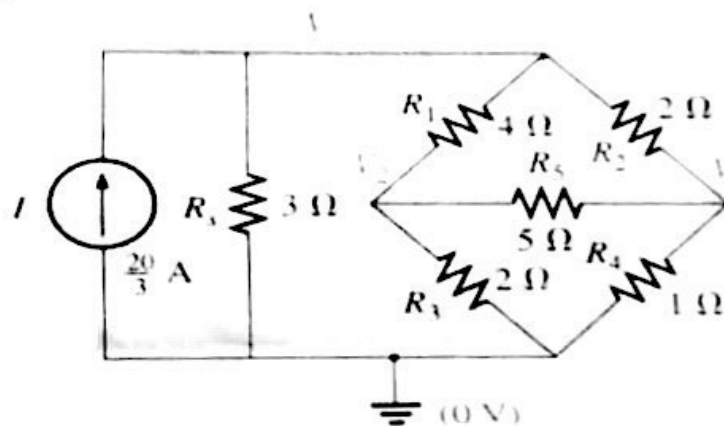- Q.1** Write down the steps of Nodal Analysis procedure. 4
- Q.2** Apply Nodal Analysis to determine current through each elements of the following figure. 6



**Class Test 3**  
**ICE 1205: Circuit Theory and Analysis**

**Time: 30 minutes**

**Marks: 10**

- Q.1** Define waveform. Show that the dc value of a sinusoidal current or voltage is  $1/\sqrt{2}$  or 0.707 of its peak value. 5
- Q.2** a. Determine the angle at which the magnitude of the sinusoidal function  $v = 10 \sin 377t$  is 4 V. 5
- b. Determine the time at which the magnitude is attained