

## Analog Electronics

### Part - A

Amplifiers: An amplifier is an electronic device that increases the voltage, current, and power of a signal.


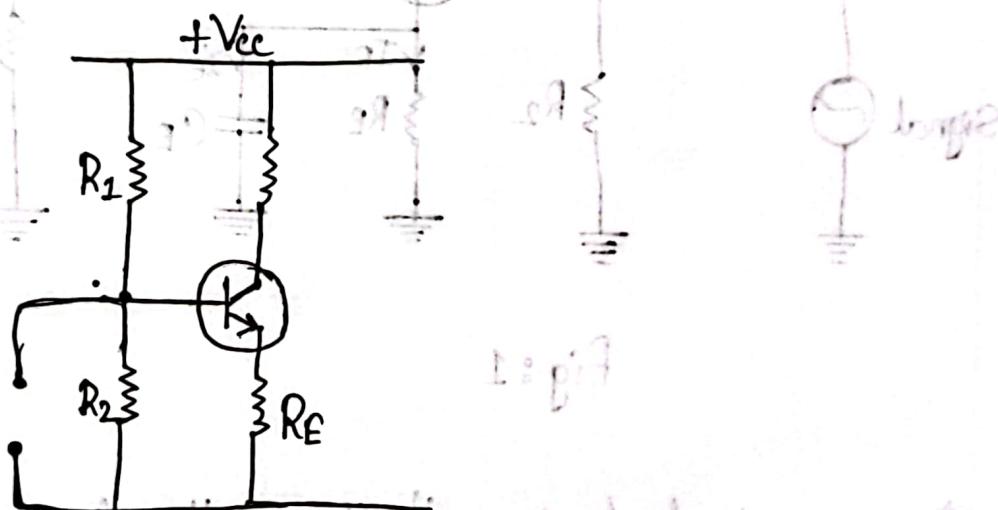



Fig: Single Stage transistor amplifier

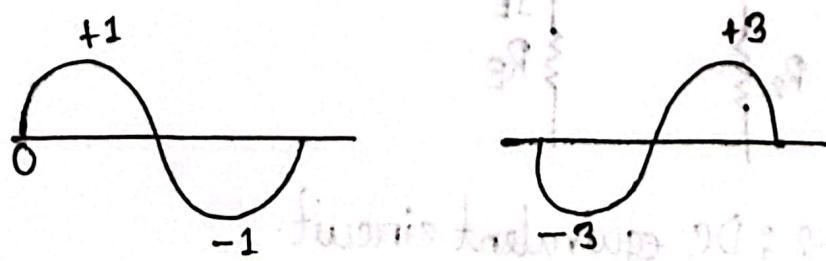Phase Reversal: The phase difference of  $180^\circ$  between the signal voltage and output voltage in a common emitter amplifier is known as phase reversal.



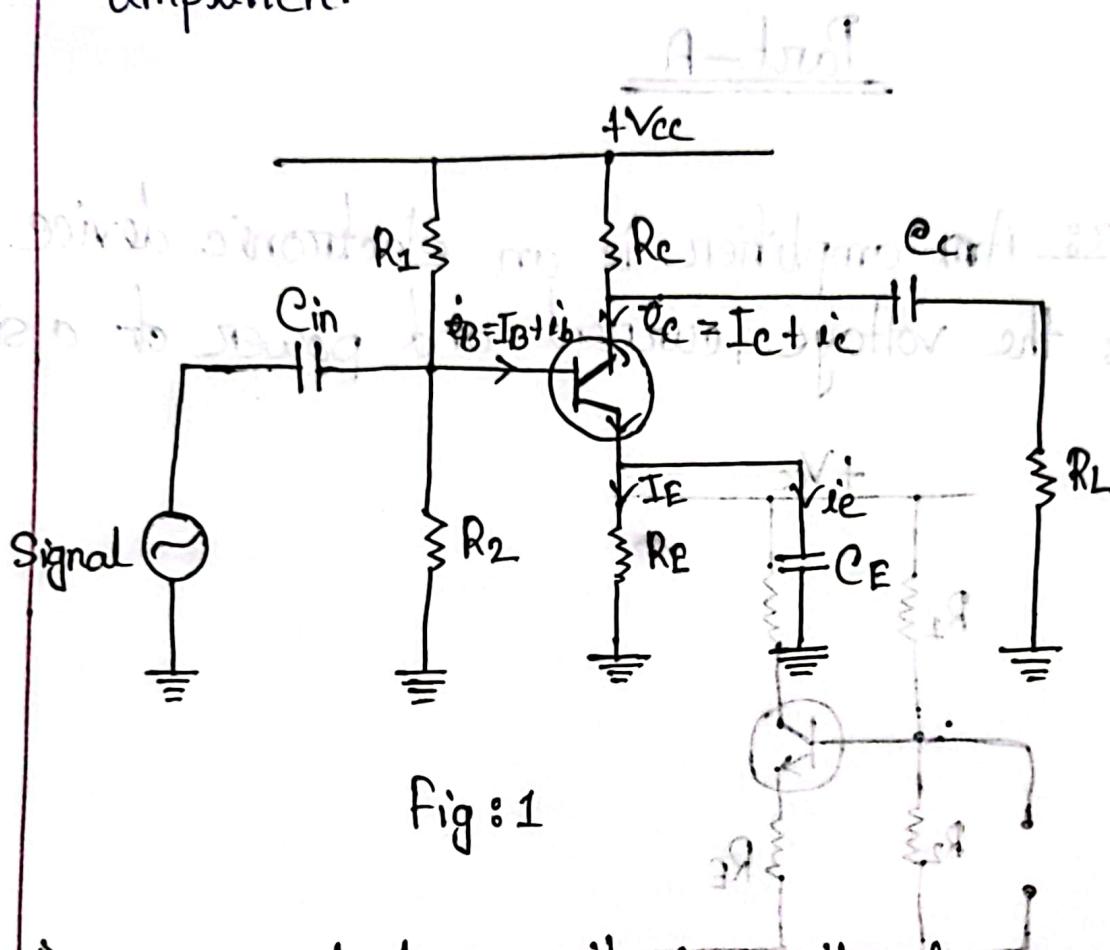13.11.22

→ Draw the DC and AC equivalent circuit of an amplifier.



D.C. equivalent circuit from the fig-1

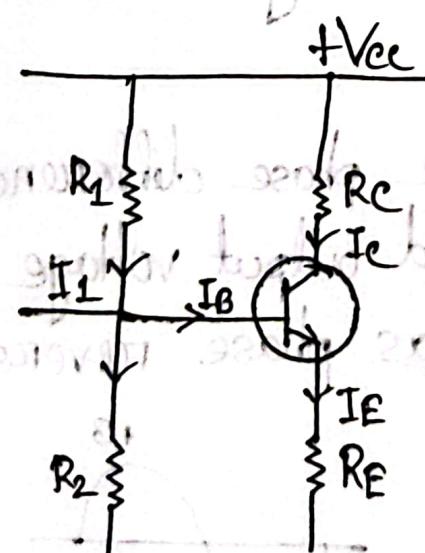


Fig-2 : DC equivalent circuit.

i) Reduce all ac sources to zero

ii) Open all the capacitors.

AC equivalent circuit from the circuit:

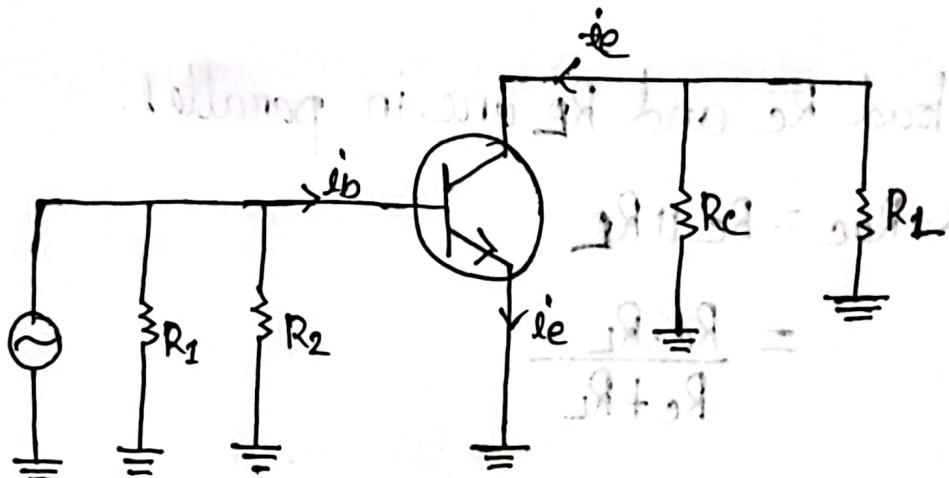


Fig-3: AC equivalent circuit

i) Reduce all dc sources to zero ( $V_{cc} = 0$ )

ii) Short all the capacitors.

Example: 10.4

① DC and AC load:


In dc load  $R_C$  and  $R_E$  are in series.

$$\therefore \text{dc load} = R_C + R_E$$

In ac load  $R_C$  and  $R_E$  are in parallel.

$$\text{AC load: } R_{ac} = R_C // R_E$$

$$= \frac{R_C \cdot R_E}{R_C + R_E}$$

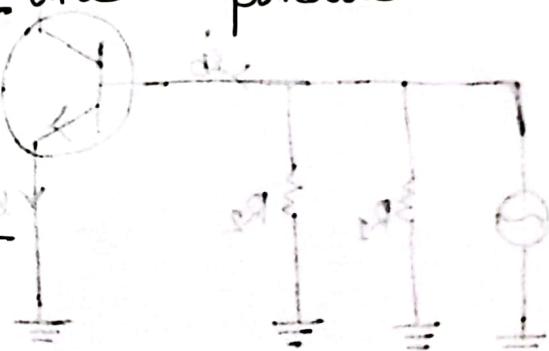

② Referring to d.c. equivalent circuit,

$$V_{ce} = V_{ee} + \frac{I_c}{R_C + R_E}$$

The maximum value will appear when  $I_c = 0$

$$\therefore V_{ce} = V_{ee}$$

The maximum collector current will flow when

$$V_{ee} = 0$$

$$\therefore \text{Maximum } I_c = \frac{V_{ee}}{R_C + R_E}$$


(iii) Maximum collector current when ac signal is applied =  $I_c$   
 maximum collector-emitter voltage =  $I_c \times R_{AC}$

Total maximum collector-emitter voltage =  $V_{CE} + I_c R_{AC}$

Maximum positive swing of ac collector current =  $\frac{V_{CE}}{R_{AC}}$

$\therefore$  Total maximum collector current =  $I_c + \frac{V_{CE}}{R_{AC}}$

AC load line :

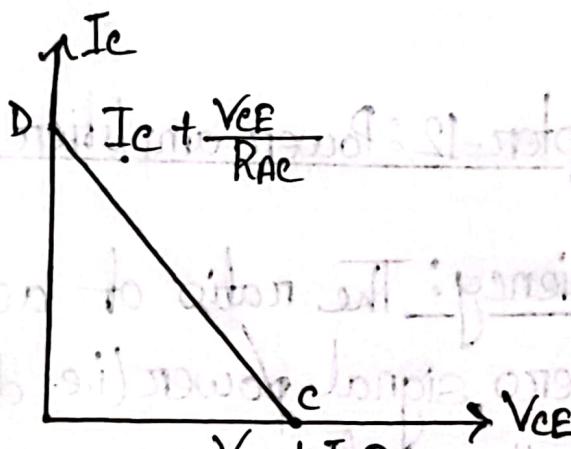

Voltage Gain:

Output voltage,  $V_{out} = i_c \cdot R_{AC}$

Input voltage,  $V_{in} = i_b \cdot R_{in}$

Voltage gain,  $A_v = \frac{V_{out}}{V_{in}}$

$$= \frac{i_c \cdot R_{AC}}{i_b \cdot R_{in}} = \beta \times \frac{R_{AC}}{R_{in}} \quad \left[ \because \frac{i_c}{i_b} = \beta \right]$$

$$\therefore \text{Power gain, } A_p = \frac{i_c^2 \cdot R_{AC}}{i_b^2 \cdot R_{in}}$$

$$= \beta^2 \times \frac{R_{AC}}{R_{in}}$$

- Explain the type of transistor amplifiers (271 page)
- Difference between voltage and power amplifier (page: 309)

### Chapter-12: Power amplifiers

① Collector efficiency: The ratio of ac output power to the zero signal power (i.e. dc power) supplied by the battery of a power amplifier is known as collector efficiency.

② Distortion: The change of output wave shape from the input wave shape of an amplifier is known as distortion.

⑩ Power dissipation capability: The ability of a power transistor to dissipate heat is known as power dissipation capability.

⑪ Class A power amplifier: If the collector current flows at all times during the full cycle of the signal, the power amplifier is known as class A power amplifier.



⑫ Class B power amplifier: If the collector current flows only during the positive half-cycle of the input signal, it is called a class B power amplifier.

⑬ Class C power amplifier: If the collector current flows for less than half-cycle of the input signal, it is called class C power amplifier.

Q

Maximum collector efficiency for class A amplifier:

19.11.22

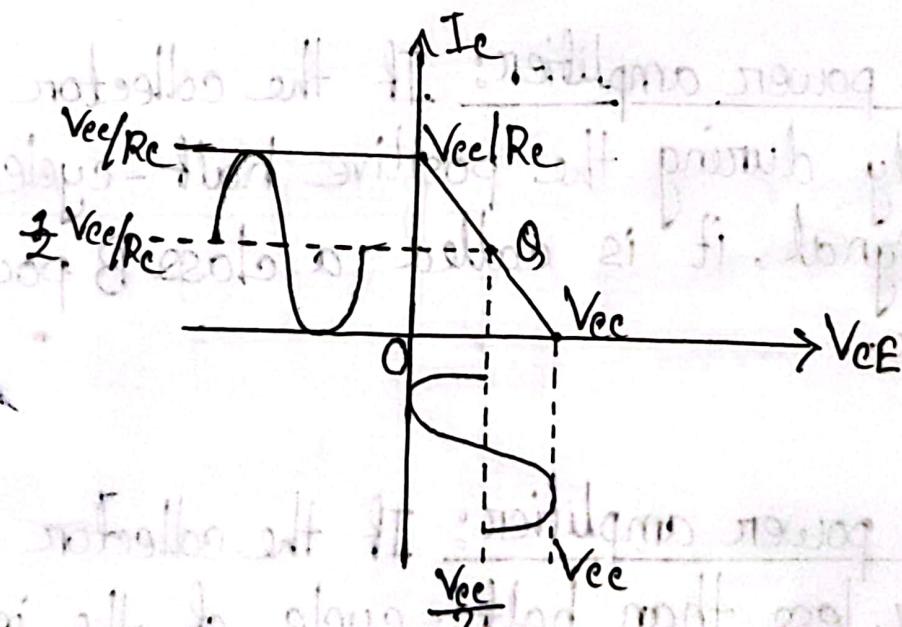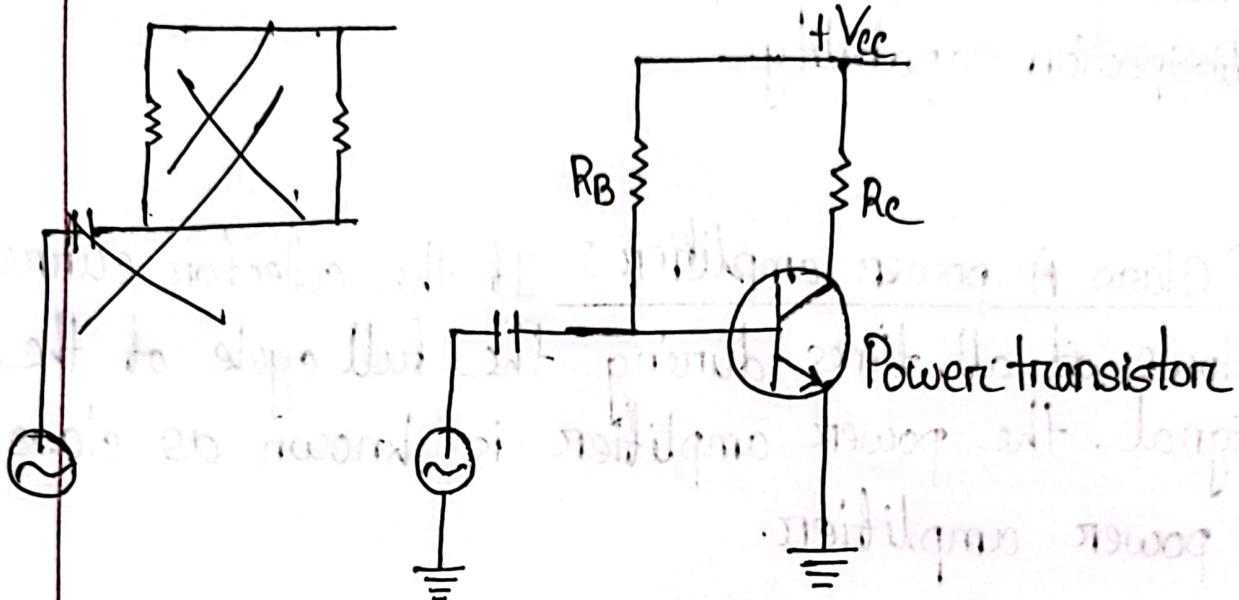

$$I_c = \frac{V_{CC}}{2R_C}$$

$$V_{EB} = \frac{V_{CC}}{2}$$

$$\text{maximum output power, } P_{o(\max)} = \frac{V_{ce}(P-P) \times I_c(P-P)}{8}$$

$$= \frac{V_{ce} \times V_{ce}/R_c}{8}$$

$$= \frac{V_{ce}^2}{8R_c}$$

$$\text{DC power input, } P_{in(dc)} = V_{ce} \times I_c \therefore$$

$$= V_{ce} \times \frac{V_{ce}}{2R_c}$$

$$= V_{ce} \frac{V_{ce}^2}{2R_c}$$

$\therefore$  Maximum collector efficiency,  $n = \frac{P_{o(\max)}}{P_{dc}} \times 100\%$

$$= \frac{V_{ce}^2}{8R_c}$$

$$= \frac{V_{ce}^2/8R_c}{V_{ce}/2R_c} \times 100\%$$


$$= 25\%$$

$$\therefore R_{rms} \text{ value} = \frac{1}{2} \left( \frac{\text{peak to peak value}}{\sqrt{2}} \right)$$

$$= \frac{1}{2} \times 0.707 \times (P-P) \text{ value}$$

20.11.22
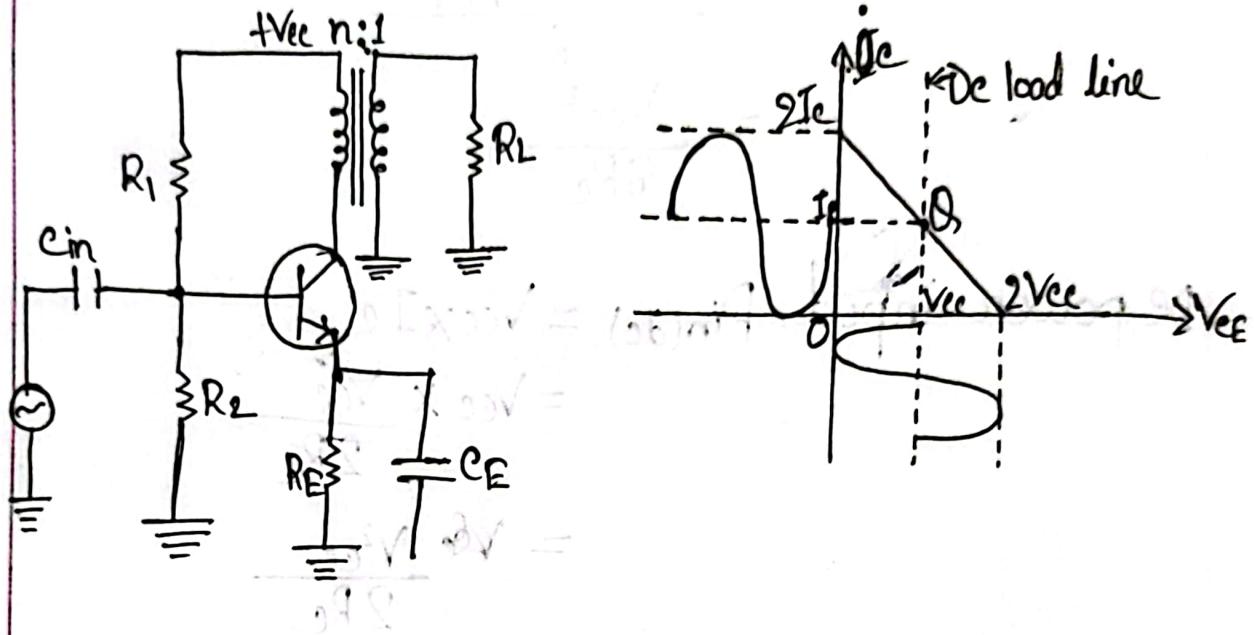
## Maximum collector efficiency of transformer coupled class A power amplifier:



$$V_{ce}(P-P) = 2V_{cc}$$

peak to peak collector current, \$i\_{c(P-P)} = 2I\_c\$

$$= \frac{V_{ce}(P-P)}{R'_L}$$

$$= \frac{2V_{cc}}{R'_L}$$

$$\begin{aligned} V_{ce} &= V_{cc} - V_T \\ 0 &= V_{cc} - V_T \\ &= V_{cc} - I_c R'_L \\ V_{cc} &= I_c R'_L \end{aligned}$$

$$\text{maximum output power: } P_o(\text{max}) = \frac{V_{cc}(P-P) \times 2I_c}{8}$$

$$\begin{aligned} &= \frac{2V_{cc} \times 2I_c}{8} \\ &= \frac{1}{2} V_{cc} I_c \\ &= \frac{1}{2} I_c^2 \cdot R'_L \end{aligned}$$

dc power input,  $P_{dc} = V_{ee} \times I_e$

$$= I_c \cdot R'_L \times I_e$$


$$= I_c^2 \cdot R'_L$$

$$\therefore \text{maximum collector efficiency} \eta = \frac{P_o(\text{max})}{P_{dc}} \times 100\%$$

$$= \frac{1/2 I_c^2 \cdot R'_L}{I_c^2 \cdot R'_L} \times 100\%$$

$$= 50\%$$

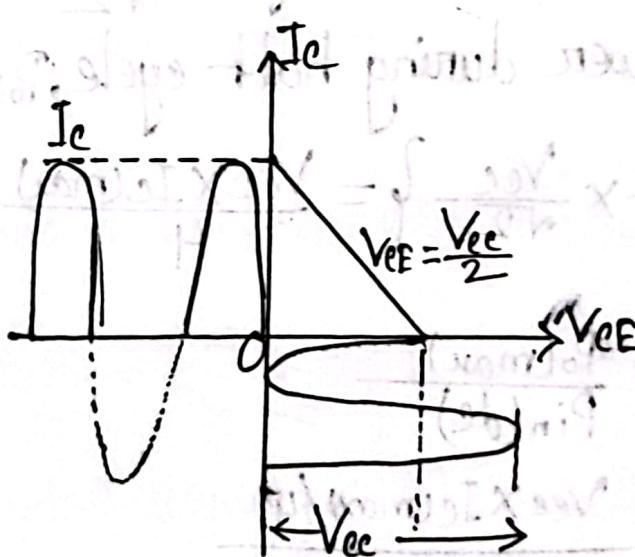Maximum efficiency for class B power amplifiers:



$$I_{dc} = \int_0^{\pi} I_c(\text{max}) \sin \theta \, d\theta$$

$$= \frac{I_c(\text{max})}{2\pi} [-\cos \theta]_0^{\pi}$$

$$= \frac{I_{c(\max)}}{2\pi} \left\{ -(\cos\pi - \cos 0) \right\}$$

$$= \frac{I_{c(\max)}}{2\pi} \times 2$$

$$= \frac{I_{c(\max)}}{\pi}$$

$$P_{dc} = \frac{V_{cc} \times I_c}{\pi}$$

$$\therefore \text{maximum collector efficiency, } \eta = \frac{P_{o(\max)}}{P_{in(dc)}}$$

$$\text{rms value of collector current} = \frac{I_{c(\max)}}{\sqrt{2}}$$

$$\text{rms value of output voltage} = \frac{V_{cc}}{\sqrt{2}}$$

ac o/p output power during half cycle,  $P_{o(\max)} =$

$$= \frac{1}{2} \left\{ \frac{I_{c(\max)}}{\sqrt{2}} \times \frac{V_{cc}}{\sqrt{2}} \right\} = \frac{V_{cc} \times I_{c(\max)}}{4}$$

$$\therefore \text{efficiency, } \eta = \frac{P_{o(\max)}}{P_{in(dc)}}$$

$$= \frac{V_{cc} \times I_{c(\max)}/4}{V_{cc} \cdot I_{c(\max)} \pi}$$

$$= \frac{\pi}{4} \times 100\% = 78.4\%$$

⇒ Difference between voltage and power amplifier.

Voltage amplifier	Power amplifier
① A voltage amplifier is designed to achieve maximum voltage amplification.	① Power amplifier is designed to obtain maximum output power.
② The transistor with high $\beta$ is used in the circuit. In other words, those transistors are employed which have thin base.	② The base is made thicker to handle larger currents. In other words, transistors with comparatively smaller $\beta$ are used.
③ $B$ range is high ( $>100$ )	③ $B$ range is low (5 to 20).
④ $R_C$ range is high ( $4-10\text{k}\Omega$ )	④ $R_C$ range is low ( $5-20\Omega$ )
⑤ Usually R-C coupling.	⑤ Invariably transformer coupling.

Power amplifier: An electronic amplifier which is designed to produce a higher magnitude signal from a given input signal is known as a power amplifier.


## Chapter-11: Multistage transistor amplifier.

Definitions: A transistor circuit containing more than one stage of amplification is known as multistage transistor amplifier.

Gains: The ratio of the output electrical quantity to the input one of the amplifier is called its gain.


$$\therefore \text{Total gain, } G_t = G_1 \times G_2 \times G_3$$

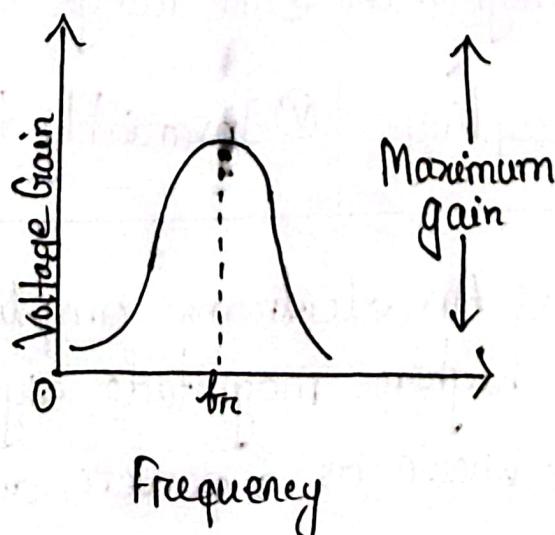Frequency response: The voltage gain of an amplifier varies with signal frequency.



Decibel gain: Power gain =  $\log_{10} \frac{P_{out}}{P_{in}}$  bel  
 $1 \text{ bel} = 10 \text{ db}$

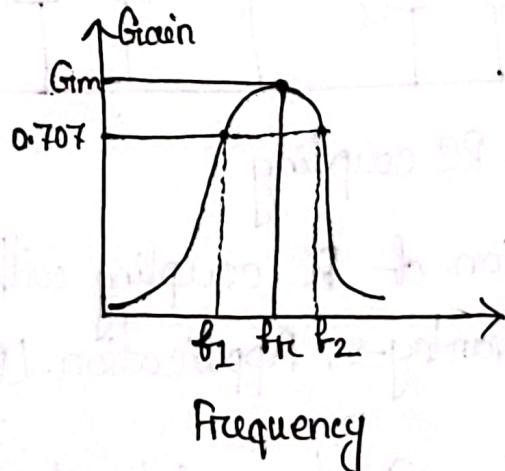Bandwidth: The range of frequency over which the voltage gain is equal to or greater than 70.7% of the maximum gain is known as bandwidth.



$$\text{Bandwidth} = f_2 - f_1 \quad [f_2 - f_1 \text{ inter frequency gap}]$$

There are three types of transistor amplifiers:

- ① RC coupling: A capacitor is used as the coupling device.
- ② Transformer coupling: transformer is used as coupling device
- ③ DC coupling: two stages maybe directly connected

## RC coupling :

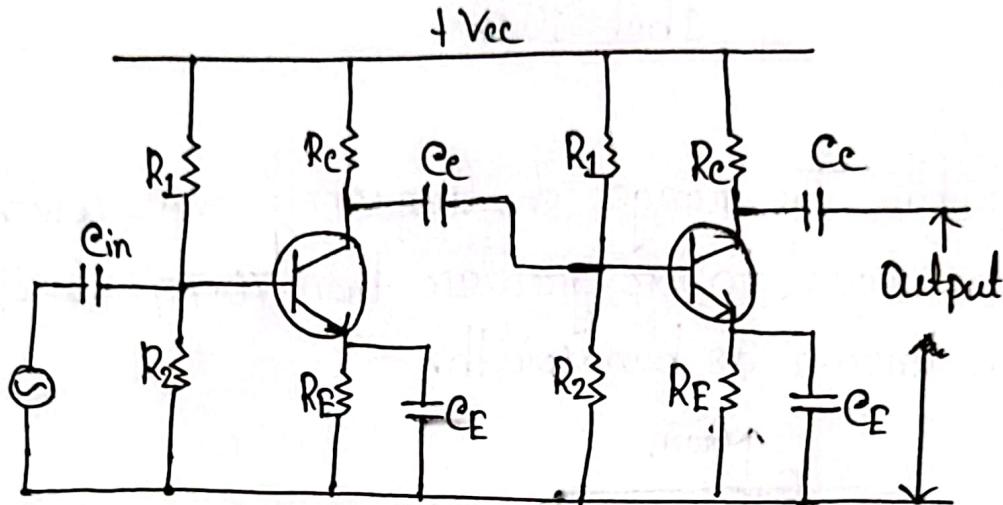


Fig - RC coupling

- ⇒ Describe operation of RC coupling with diagram.
- ⇒ Advantages, disadvantages, Application. (Pag - 290)

Collector — Supply — 1st coil

Base — resistor — 2nd coupling

## Transformer coupling :

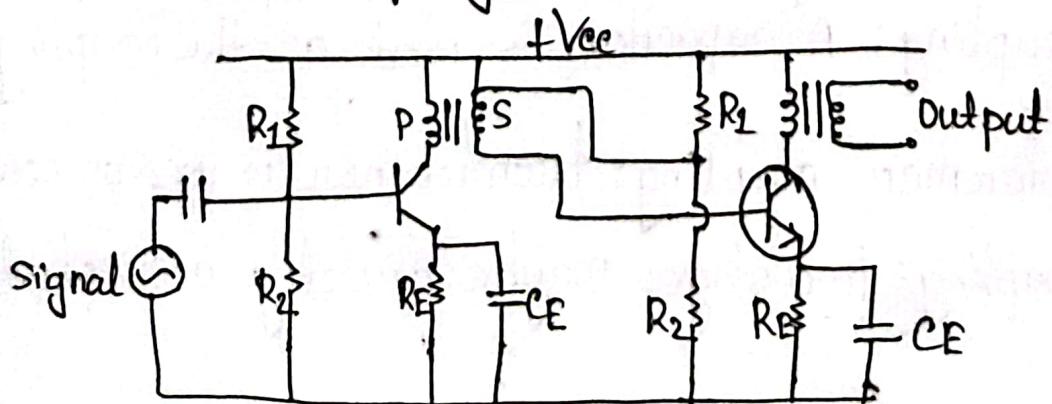


Fig - Transformer coupling

The load  $R'_L$  appearing on the primary side will be:

$$R'_L = \left(\frac{N_p}{N_s}\right)^2 \times R_L$$

→ Math: 11.16, 11.17 (page - 297)

→ Comparison of different types of coupling (301 page)

→ 1st question 2nd yr math must.

## Feedback Amplifiers:

Feedback amplifier: The process of sending part of the output signal of an amplifier back to the input of the amplifier is called feedback.

There are four types of feedback amplifiers.

### 1. Voltage series feedback:

$$\text{Gain, } A_{\text{Vsf}} = \frac{A_{\text{v}}}{1 + BA_{\text{v}}}$$

### 2. Current series feedback:

$$\text{Voltage gain, } A_{\text{Vsf}} = \frac{-R_L}{R_E}$$

### 3. Voltage shunt feedback:

$$\text{Voltage gain, } A_{\text{Vsf}} = A_v \frac{R_f}{R_s + R_f}$$

### 4. Current shunt feedback:

$$\text{Voltage gain, } A_{\text{Vsf}} = A_v \left[ \frac{R_f}{R_f + R_s} \right]$$

Positive feedback: When the feedback voltage is so applied that it increases the input voltage (or current) i.e. it is in phase with the input, it is called as positive feedback or regenerative or direct feedback.

$$\text{Amplifier gain } A_f = \frac{A}{1+BA}$$

Negative feedback: When the feedback voltage (or current) is so applied that it decreases the input voltage (or current) it is out of phase with the input it is called as negative or degenerative or direct feedback.

$$\text{Amplifier gain, } A_f = \frac{A}{1+BA}$$

⇒ What are the effects of negative feedback?

(i) Increasing stability: The gain of the amplifier with negative feedback is given by  $A' = \frac{A}{1+BA}$ .

In negative feedback amplifiers, the designer deliberately makes the product  $BA$  much greater than unity so that  $1$  may be neglected in comparison to it. Hence,

$$A' \equiv \frac{A}{BA} \approx \frac{1}{B}$$

Thus  $A'$  depends only on  $B$  (feedback ratio) i.e. characteristics of feedback circuit. As feedback circuit is usually a voltage divider (resistive network) and resistors can be selected very precisely with almost zero temperature coefficient of resistance, therefore the gain is unaffected by changes in temperature, variations in transistor parameters and frequency. Hence the gain of the amplifier is extremely stable.

(II) Reduction in non-linear distortion: A large signal stage has non-linear distortion because its voltage gain changes at various points in the cycle. The use of negative feedback in large signal amplifiers reduces the non-linear distortion.

2)

Let,  $D$  = Distortion voltage generated in amplifier without feedback.

$D'$  = Distortion voltage generated in amplifier with feedback.

Suppose,  $D' = Dx$

Fraction of output distorted voltage feedback to input =  $B D' = BDx$

Amplified distorted voltage =  $BxDA$

$$D' = D - BxDA$$

$$Dx = D - BxDA$$

$$Dx = D(1 - BxA)$$

$$x = 1 - BxA$$

$$x + BxA = 1$$

$$x(1 + BxA) = 1$$


$$x = \frac{1}{1 + BxA}$$

$$Dx = \frac{D}{1 + BxA}$$

$$D' = \frac{D}{1 + BxA}$$

So the negative feedback reduces the amplifier distortion by a factor  $(1 + BA)$ .

### (III) Increased bandwidth:

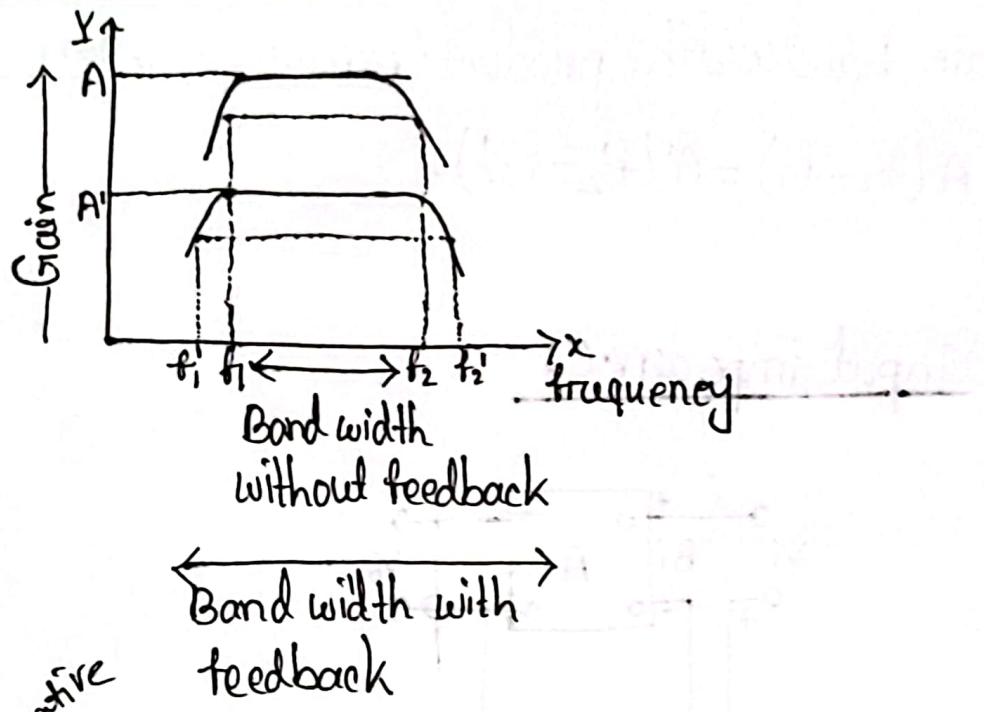

When <sup>negative</sup> feedback is applied, the gain of the amplifier is decreased but gain bandwidth remains the same. This indicates that the bandwidth must increase to compensate the decrease in gain. It can be shown that with negative feedback, the lower and upper 3dB frequencies are expressed as,

$$f_1' = \frac{f_1}{(1+BA)} \quad \text{--- } ①$$

$$f_2' = f_2 (1+BA) \quad \text{--- } ②$$

These frequencies are shown in figure (2). It is clear from expression (1) and (2) that  $f_1'$  decreases while

$f_2'$  increases. Thus the bandwidth increases, of course gain bandwidth product remain the same i.e.

$$A(f_2 - f_1) = A'(f_2' - f_1').$$

#### (IV) Input impedance:

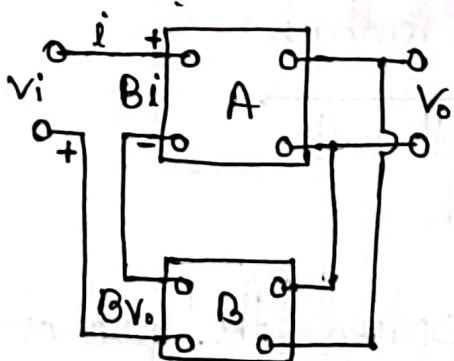


Fig: Input impedance increases due to negative feedback

In order to consider the effect of feedback on input impedance of a transistor amplifier, we assume that  $A$  is the normal gain of the amplifier without feedback.  $Bv_o$  is the fraction of the output voltage which is feedback to the input terminals as shown in fig. Without feedback the input impedance is


$$Z_i = \frac{e_1}{i_1} = \frac{v_1}{i_1} \quad (v_1 = e_1)$$

With feedback the input impedance  $Z_{if}$  is given by,

$$\begin{aligned}
 Z_{if} &= \frac{e_1 - BV_o}{i_1} \\
 &= \frac{V_1 - BV_o}{I_1} \\
 &= \frac{V_1 - BA V_1}{I_1} \\
 &= \frac{e_1 - B \times A e_1}{I_1} \quad [ \because V_o = A e_1 ] \\
 &= \frac{e_1}{I_1} (1 - BA) \\
 &= Z_i (1 - AB)
 \end{aligned}$$

In negative feedback (~~positive~~  $(1 - AB)$ ) is greater than unity and consequently,  $Z_{if}$  is greater than  $Z_i$ . That is, due to negative feedback, input impedance of a transistor amplifier increases.

### (v) Output impedance:

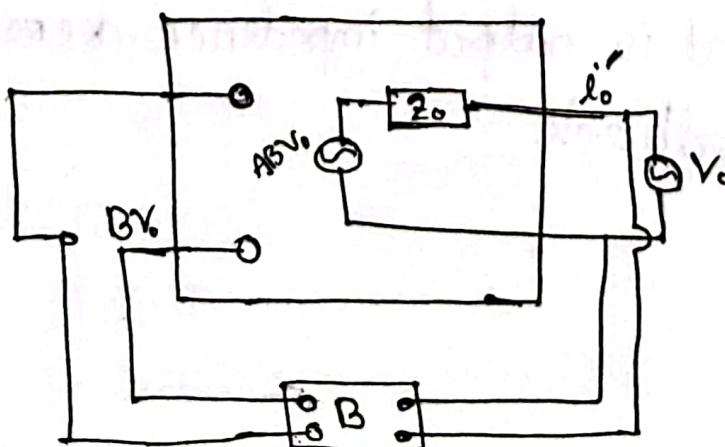

The output impedance without feedback,  
 $Z_o = \frac{V_o}{i_o}$

95

In order to find ~~the~~ out the output impedance of the amplifier with feedback, we short circuit the source and connect a voltage source  $V_o$  at the output terminals as show in fig. The output has been replaced by an equivalent voltage source  $A B V_o$ . Let  $i_o'$  be the current with feedback.

From figure,

$$Z_o i_o' = V_o - A B V_o$$

$$\Rightarrow i_o' = \frac{V_o - A B V_o}{Z_o}$$

$$= \frac{V_o}{Z_o} (1 - A B)$$

So the output impedance is,

$$Z_{o f} = \frac{V_o}{i_o'} = \frac{Z_o}{1 - A B}$$

since the negative feedback  $(1 - A B) > 1$ .  $Z_{o f}$  is less than  $Z_o$ . That is output impedance decreases due to negative feedback.

Example-1:

When the negative feedback is applied to an amplifier of gain 100, the overall gain falls to 50. calculate.

- ① the fraction of output voltage feedback.
- ② if this fraction is maintained, the value of the amplification required if the overall stage gain is to be 75.

(I) Solution: Give that,

$$A' = 50$$

$$A = 100$$

$$A' = \frac{A}{1+BA}$$

$$50 = \frac{100}{1+100B}$$

$$\Rightarrow 50 + 5000B = 100$$

$$\Rightarrow 5000B = 100 - 50$$

$$\Rightarrow B = \frac{100 - 50}{5000} = 0.01$$

(II) Solution:  $A' = 75$

$$B = 0.01$$

$$A' = \frac{A}{1+BA}$$

$$\Rightarrow 75 = \frac{A}{1+0.01A}$$

$$\Rightarrow 75 = A - 0.75A$$

$$\Rightarrow A(1 - 0.75) = 75$$

$$\Rightarrow A = \frac{75}{0.25}$$

$$\therefore A = 300$$

Example-2: The gain of the amplifier without feedback is 50 whereas with negative feedback it falls to 25. If due to ageing, the amplifier gain falls to 40, find the percentage reduction in stage gain (i) without feedback and (ii) with negative feedback.

(i) Solution: % reduction in stage gain =  $\frac{50-40}{50} \times 100\% = 20\%$

(ii) Solution:

$$A' = \frac{A}{1+AB}$$

$$\Rightarrow 25 = \frac{50}{1+50B}$$

$$\Rightarrow B = \frac{50-25}{1250} = \frac{1}{50} = 0.02$$

$$\text{with negative feedback} = \frac{A}{1+BA} = \frac{40}{1+40 \times 0.02} = 22.2$$

$$\therefore \% \text{ reduction in stage gain} = \frac{25-22.2}{25} \times 100\% = 11.2\%$$

Example-3: A transistor amplifier has a voltage gain of 50. The input resistance of the amplifier is  $1k\Omega$  and the output resistance is  $40k\Omega$ . The amplifier is now provided with 10% negative voltage feedback in series with the input. Calculate the voltage gain, input, output resistance with the feedback.

(I) Solution: 10% negative feedback has been provided

$$B = \frac{-10}{100} = -0.1$$

$$A' = \frac{A}{1 - (-BA)} = \frac{50}{1 + 0.1 \times 50}$$

$$= \frac{50}{6} = 8.33$$

(II) Solution:

$$\text{Input resistance, } Z_{if} = Z_i(1 - BA)$$

$$= 1 \times (1 + 0.1 \times 50)$$

$$= 1 \times 6$$

$$= 6k\Omega$$


(III) Solution:

$$\text{Output resistance, } Z_{of} = \frac{Z_o}{1 - AB} = \frac{40}{1 + 5}$$

$$= \frac{40}{6} = 6.66k\Omega$$

29

## Voltage Series feedback:

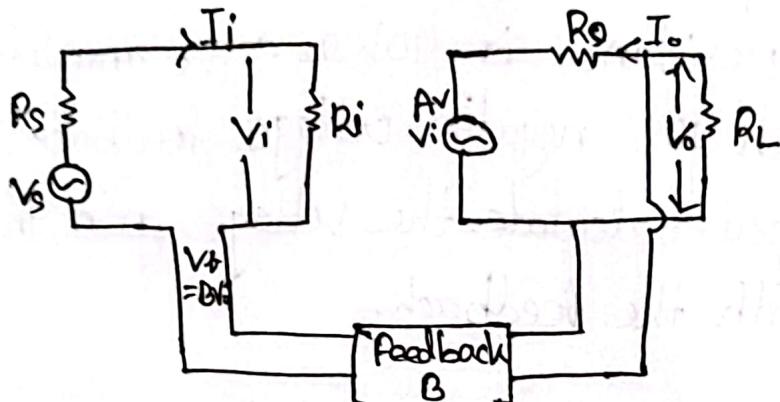

From the input circuit,

$$V_s - V_i - V_f = 0$$

$$\begin{aligned} V_s &= V_i + V_f \\ &= V_i + B V_o \quad [V_f = B V_o] \end{aligned}$$

$$\begin{aligned} \text{Voltage gain, } A_{vf} &= \frac{V_o}{V_s} \\ &= \frac{V_o}{V_i + B V_o} \\ &= \frac{A_v V_i}{V_i (1 + B A_v)} \\ \therefore A_{vf} &= \frac{A_v}{1 + B A_v} \end{aligned}$$

### Input resistance:

$$R_{if} = \frac{V_s}{I_i} \text{ V}$$

from input circuit,

$$V_s - V_i - V_f = 0$$

$$V_s = V_i + V_f$$

$$= V_i + B V_o$$

$$\therefore R_{if} = \frac{V_i + B V_o}{I_i}$$

$$= \frac{V_i + B \cdot A_v \cdot V_i}{I_i} \quad [V_o = A_v \cdot V_i]$$

$$= \frac{V_i}{I_i} (1 + BA_v)$$

$$= R_i (1 + BA_v)$$

### Output resistance:

$$R_{of} = \frac{V_o}{I_o} \text{ V}$$

from output circuit,  $V_o - I_o R_o - A_v V_i = 0 \quad \text{--- (1)}$

$$V_s - V_i - B V_o = 0$$

Considering  $V_s = 0$

$$-V_i = B V_o$$

$$\therefore V_i = -B V_o$$

3)

putting the value of (iii)  $v_i$  in eqn(i),

$$V_o - I_o R_o - A_v (-B V_o) = 0$$

$$\Rightarrow V_o - I_o R_o + A_v B V_o = 0$$

$$\Rightarrow V_o (1 + A_v B) = I_o R_o$$

$$\Rightarrow \frac{V_o}{I_o} = \frac{R_o}{(1 + A_v B)}$$

$$\Rightarrow R_{af} = \frac{R_o}{1 + A_v B}$$

Part : BOperational amplifier

Question-1: What is operational amplifier?

Answer: An operational amplifier is a circuit that can perform such mathematical operations as addition, subtraction, integration and differentiation.

Question-2: Write down the application of op-amp.


Answer: Operational amplifier has many different applications.

They are:

- ① As inverting amplifier
- ② As non-inverting amplifier
- ③ As differentiator
- ④ As integrator
- ⑤ As phase shifter
- ⑥ As scale changer
- ⑦ As adder or summing amplifier
- ⑧ As voltage or current converter.

37
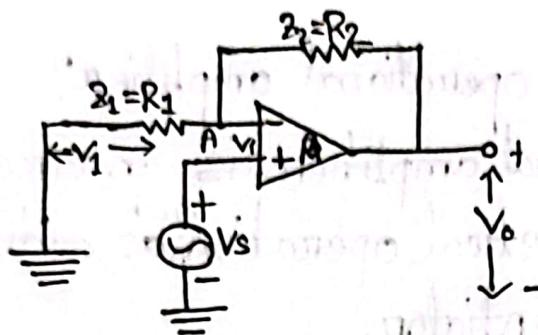
## Voltage gain of non-inverting amplifier:



If we assume that we are not at saturation, the potential at point A is the same as:  $V_{in}$ . Since the input impedance of op-amp is high. All of the current that flows through  $R_2$  also flows through  $R_1$ . We have

$$\text{Voltage across } R_1 = V_{in} - 0$$

$$\text{u u } R_2 = V_{out} - V_{in}$$

Now,

$$A = \frac{V_o}{V_i - V_s}$$

$$\Rightarrow V_i - V_s = \frac{V_o}{A}$$

$$\Rightarrow V_i - V_s = 0$$

$$\Rightarrow V_i = V_s$$

$$V_i = \frac{V_o}{R_1 + R_2} \cdot R_1$$


$$V_1 = V_S = \frac{V_o}{R_1 + R_2} \times R_2$$

$$\therefore V_S = \frac{V_o \cdot R_1}{R_1 + R_2}$$

$$\Rightarrow \frac{V_S}{V_o} = \frac{R_1}{R_1 + R_2} \Rightarrow \frac{V_o}{V_S} = \frac{R_1 + R_2}{R_1}$$

$\therefore A = 1 + \frac{R_2}{R_1}$  which is the gain of a non-inverting operational amplifier.

Voltage gain of an inverting op-amp:

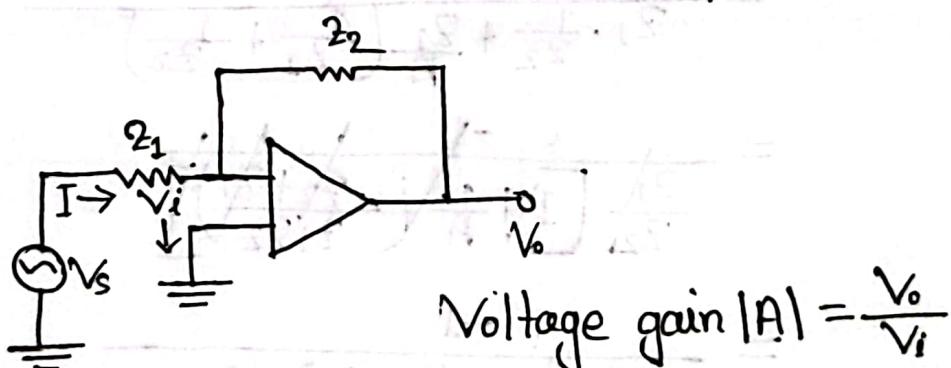

Current  $I$  flowing through  $Z_1$  will also flow through  $Z_2$ .

Thus current through  $Z_1$  is  $I = \frac{V_s - V_i}{Z_1}$

Current through  $Z_2$  is  $I = \frac{V_i - V_o}{Z_2}$

$$\therefore \frac{V_s - V_i}{Z_1} = \frac{V_i - V_o}{Z_2}$$

$$\Rightarrow \frac{V_s}{Z_1} - \frac{V_i}{Z_1} = \frac{V_i}{Z_2} - \frac{V_o}{Z_2}$$

35


$$\begin{aligned}
 \Rightarrow \frac{V_o}{Z_2} &= \frac{V_i}{Z_2} + \frac{V_i}{Z_1} - \frac{V_s}{Z_1} \\
 \Rightarrow \frac{V_o}{Z_2} &= V_i \left( \frac{1}{Z_2} + \frac{1}{Z_1} \right) - \frac{V_s}{Z_1} \\
 \Rightarrow \frac{V_o}{Z_2} &= \frac{-V_o}{A} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right) - \frac{V_s}{Z_1} \quad [\text{since } A = \frac{-V_o}{V_i} \text{ so } V_i = -\frac{V_o}{A}] \\
 \Rightarrow \frac{V_o}{Z_2} + \frac{V_o}{A} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right) &= -\frac{V_s}{Z_1} \\
 \Rightarrow V_o \left\{ \frac{1}{Z_2} + \frac{1}{A} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right) \right\} &= -\frac{V_s}{Z_1} \\
 \Rightarrow \frac{V_o}{V_s} &= \frac{-1}{Z_1 \left[ \frac{1}{Z_2} + \frac{1}{A} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right) \right]} \\
 &= \frac{-1}{Z_1 \cdot \frac{1}{Z_2} + \frac{Z_1}{A} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right)} \\
 &= \frac{-1}{\frac{Z_1}{Z_2} \left[ 1 + \frac{1}{A} \left( \frac{Z_1 + Z_2}{Z_1 Z_2} \right) \right]} \\
 &\underline{\underline{\frac{-1}{Z_1 \cdot \frac{1}{Z_2} + \frac{Z_1}{A} \left( \frac{Z_1 + Z_2}{Z_1 Z_2} \right)}}} \\
 &= \frac{-1}{\frac{Z_1}{Z_2} \left[ 1 + \frac{1}{A} \left( 1 + \frac{Z_2}{Z_1} \right) \right]}
 \end{aligned}$$

~~$\frac{-1}{Z_1 \cdot \frac{1}{Z_2} + \frac{Z_1}{A} \left( \frac{Z_1 + Z_2}{Z_1 Z_2} \right)}$~~

$$\therefore \frac{V_o}{V_s} = -\frac{Z_2}{Z_1}$$

which is the gain of inverting op-amp.

→ Differential amplifier:

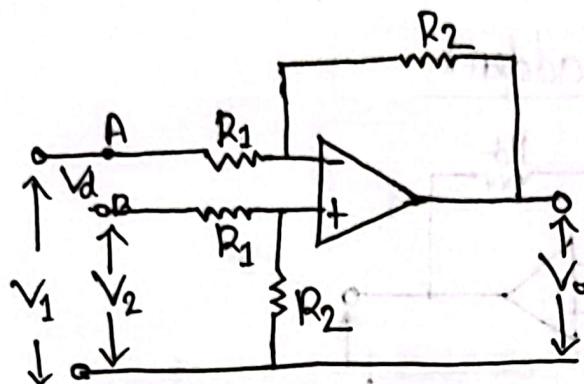

The voltage  $e_2 = \left(\frac{R_2}{R_1+R_2}\right)V_2$ . Here  $\frac{R_2}{R_1+R_2}$  is termed as the transfer function  $T(s)$  of the network involving  $R_1$  and  $R_2$  at the terminal 2. Similarly by the principle of superposition, the voltage at the inverting input terminal 1, is

$$e_1 = \left(\frac{R_2}{R_1+R_2}\right) \cdot V_1 + \left(\frac{R_1}{R_1+R_2}\right) \cdot V_o$$

$$e_1 = e_2$$

$$\left(\frac{R_2}{R_1+R_2}\right) \cdot V_1 + \left(\frac{R_1}{R_1+R_2}\right) \cdot V_o = \left(\frac{R_2}{R_1+R_2}\right) V_2$$

$$\Rightarrow \frac{1}{R_1+R_2} (R_2 V_1 + R_1 V_o) = \frac{1}{R_1+R_2} (R_2 \cdot V_2)$$

$$\Rightarrow R_2 V_1 + R_1 V_o = R_2 V_2$$

$$\Rightarrow R_1 \cdot V_o = R_2 \cdot V_2 - R_2 \cdot V_1$$


$$\Rightarrow R_2 \cdot V_o = R_2 (V_2 - V_1)$$

$$\therefore V_o = \frac{R_2}{R_1} (V_2 - V_1) = \frac{R_2}{R_1} \cdot V_d$$

[Here,  $V_2 - V_1 = V_d$ ]

## Application of operational amplifier:

### ① Summing amplifier/adder:

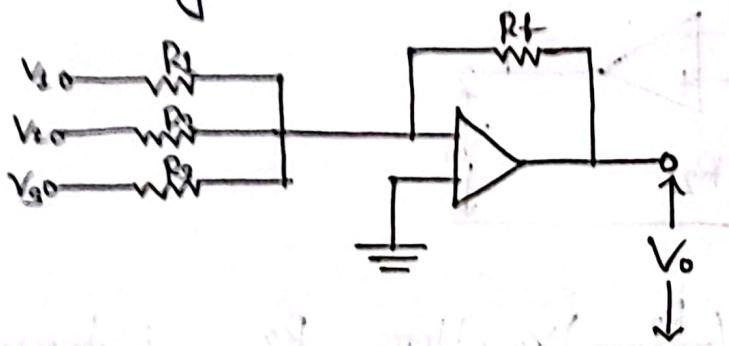

It is the same as the inverting amplifier except that it has several input terminals. Virtual ground exists at the inverting terminal due to feedback and the input current to the ideal amplifier is zero. Thus the current equation for the node at the inverting terminal is,

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_o}{R_f}$$


$$\Rightarrow \left\{ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right\} R_f = -V_o$$

$$\Rightarrow \left\{ \frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R} \right\} R_f = -V_o \quad [\text{if } R_1 = R_2 = R_3 = R]$$

$$\Rightarrow \frac{R_f}{R} (V_1 + V_2 + V_3) = -V_o$$

$$\therefore V_o = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

⑪ Integrator:

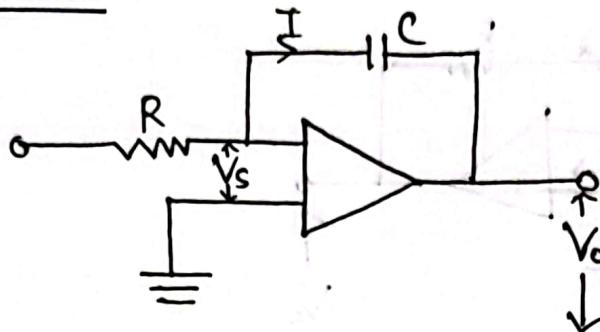

In this inverting amplifier feedback resistor  $R_2$  is replaced by a capacitor  $C$ . Feedback through the capacitor forces a virtual ground to exist at the inverting input terminal. It means voltage across  $C$ ,  $\dot{q}$ , is simply the output voltage  $V_o$ . We can write,

$$\begin{aligned} V_o(t) &= \frac{-q}{C} \\ &= -\frac{q}{C} \\ &= -\frac{1}{C} \int I dt \end{aligned} \quad \left| \begin{array}{l} I = \frac{dq}{dt} \\ dq = Idt \\ q = \int I dt \end{array} \right.$$


Input current to the ideal amplifier is zero

$$I = \frac{V_s(t)}{R}$$

$$\therefore V_o(t) = -\frac{1}{C} \int \frac{V_s(t)}{R} dt \quad [\text{keeping the value of } I]$$

$$\therefore V_o(t) = \frac{-1}{CR} \int V_s(t) dt$$

### (III) Differentiator:

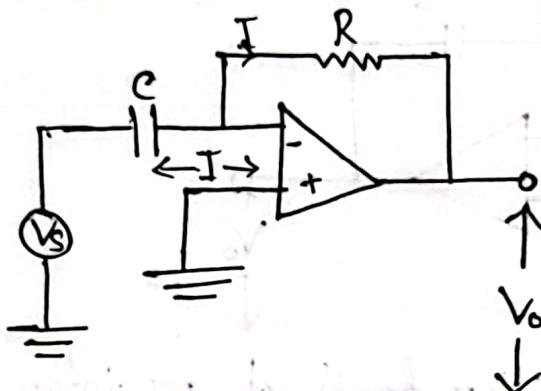

In inverting operation amplifier, we replace the input resistance by a capacitor to design a differentiator. Because of virtual ground at the inverting terminal, we have,

$$\begin{aligned} I &= \frac{dq}{dt} \\ &= \frac{d}{dt}(CV_s) \\ &= C \frac{dV_s}{dt} \end{aligned}$$


\* The output voltage,

$$\begin{aligned} V_o &= -IR \\ &= -RC \frac{dV_s}{dt} \end{aligned}$$


**IV Comparator:** The function of voltage comparator is to compare function the time varying voltage at one input with a fixed reference voltage on the other.



$e_i$  = Variable  
 $e_R$  = fixed

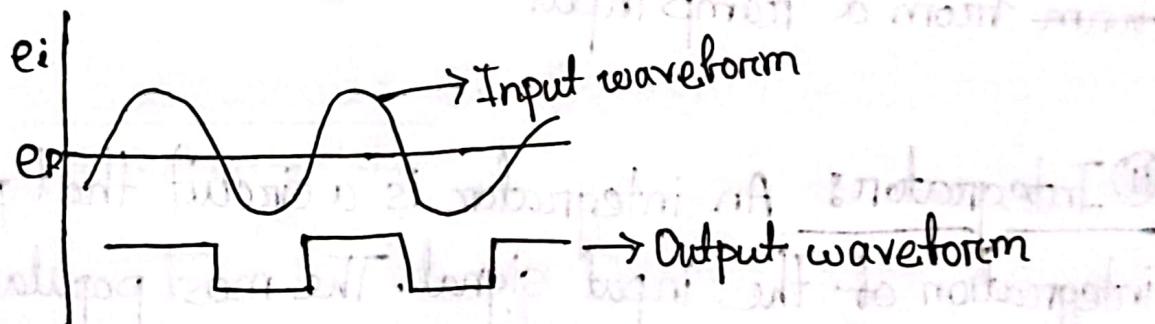

## **V Schmitt trigger:**

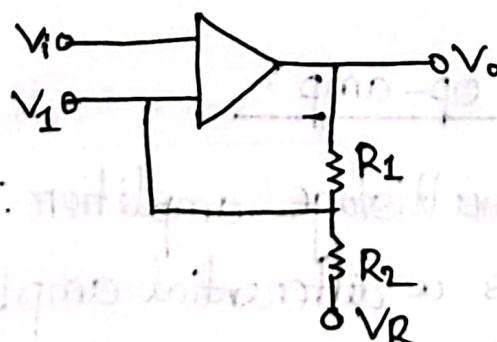

(a) For  $V_i < V_1$  and  $V_o = +V_o$

$$V_1 = \left( \frac{R_1}{R_1+R_2} \right) V_R + \left( \frac{R_2}{R_1+R_2} \right) V_o$$

(b) For  $V_i > V_1$

$$V_2 = \left( \frac{R_1}{R_1+R_2} \right) V_R - \left( \frac{R_2}{R_1+R_2} \right) V_o$$

X

① Differentiator: A differentiator is a circuit that performs differentiation of the input signals. A differentiator produces an output voltage that is proportional to the rate of change of the input voltage. Its important application is to produce a rectangular output form from a ramp input.

② Integrator: An integrator is a circuit that performs integration of the input signal. The most popular application of an integrator is to produce a ramp output voltage.

→ Characteristics of op-amp:

- ① An op-amp is a multistage amplifier. The input stage of an op-amp is a differential amplifier stage.
- ② An inverting input and non-inverting output.
- ③ A high input impedance at both input.
- ④ A low output impedance ( $<200\Omega$ )

- ⑤ A large open-loop voltage gain.
- ⑥ The voltage gain remain constant over a wide frequency range.
- ⑦ Very large CMRR ( $> 90\text{dB}$ ).

Input Bias current: In the real world, tiny amounts of current actually do flow into both the inverting and non-inverting input of the components. These currents are referred to as the input bias currents.

$$I_{\text{bias}} = \frac{I_{D_1} + I_{D_2}}{2}$$

Input offset current: Input offset current is the difference of the currents into the two terminals with the output at zero voltage.

$$I_{\text{ID}} = I_{D_1} - I_{D_2}$$

$$I_{\text{ID}} = |I_{D_1} - I_{D_2}|$$

Q3

Input offset voltage: Input offset voltage is defined as the voltage that must be applied between the two input terminals of the op-amp to obtain zero volts at the output.

Slew rate: The slew rate is defined as the maximum rate of output voltage change per unit time.

$$\text{Slew rate, } S = \left( \frac{dV_o}{dt} \right)_{\text{max}}$$

The unit of slew rate is volt/ $\mu$ s.

Common mode rejection ratio: Common mode rejection ratio is the measure of a device's ability to reject the signal common to both the positive and negative device input.

$$CMRR = \frac{A_d}{A_c} = \frac{\text{Differential gain}}{\text{Common mode gain}}$$

## Transistor Oscillators

Oscillators: Oscillator may be defined as a circuit which generates an a.c. output signal without any externally applied input signal or a circuit which converts d.c. energy into a.c. energy at very high frequency.

Essential components of oscillator are:

① Tank circuit: The tank circuit of an inductance coil in parallel with a capacitor. The frequency of oscillation in the circuit depends upon the values of inductance and capacitance. This is given by:


$$f = \frac{1}{2\pi\sqrt{LC}}$$

② Transistor amplifier: It receives dc power from the battery and changes it into ac power for supplying it to the tank circuit. The oscillations

AS

of tank circuit are feed to the transistor amplifier which are amplified due to transistor amplifying action.

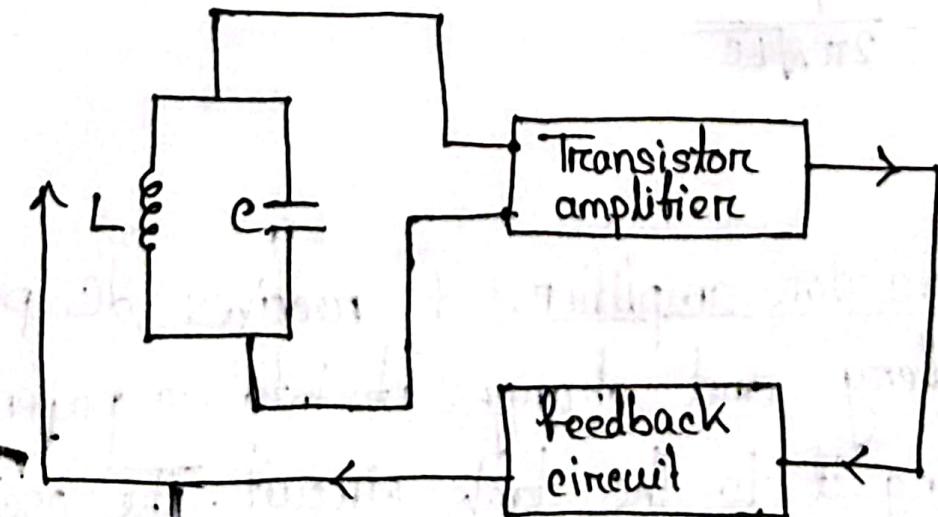(iii) Feed Feedback circuit: The feedback ~~circuit~~ circuit supplies a part of the output energy to tank circuit in correct phase to overcome the losses occurring in the tank circuit and the balance is radiated out in the form of electromagnetic waves. The feedback circuit provides a positive feedback.



## Hartley Oscillator:

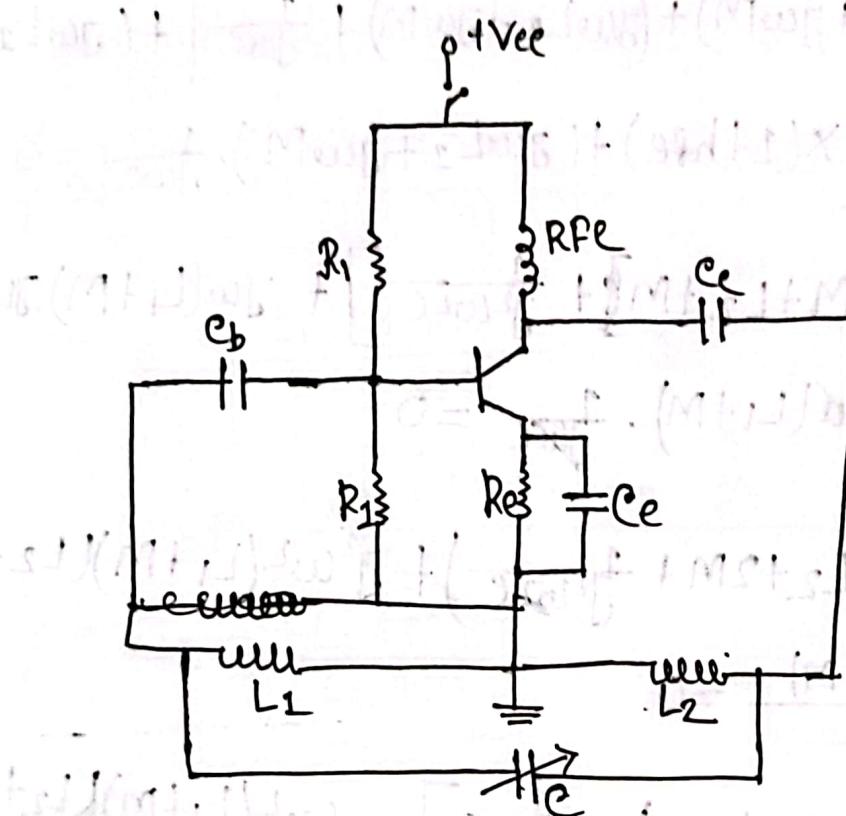


fig-a : Shunt-feed hartley oscillator

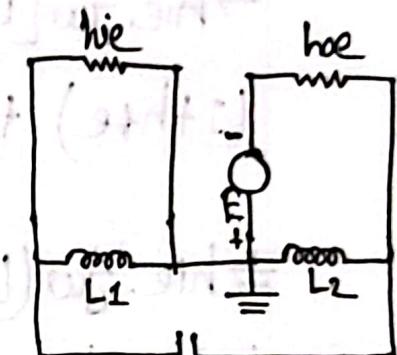


fig-b: Equivalent circuit

The general equation of the oscillator:

$$h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 (1 + h_{fe}) + z_1 z_3 = 0 \quad \text{--- (1)}$$

$$\text{Here, } z_1 = j\omega L_1 + j\omega M,$$

$$z_2 = j\omega L_2 + j\omega M$$

$$z_3 = \frac{1}{j\omega C}$$

Substituting the values into equation (1),

$\alpha^2$

$$hie(z_1 + z_2 + z_3) + z_1 z_2 (1 + hfe) + z_1 z_3 = 0$$

$$\Rightarrow hie \left[ (j\omega L_1 + j\omega M) + (j\omega L_2 + j\omega M) + \frac{1}{j\omega c} \right] + (j\omega L_1 + j\omega M)$$

$$(j\omega L_2 + j\omega M) \times (1 + hfe) + (j\omega L_1 + j\omega M) \cdot \frac{1}{j\omega c} = 0$$

$$\Rightarrow hie \cdot j\omega \left[ L_1 + M + L_2 + M \right] + \frac{j}{j^2 \omega^2 c} + j\omega(L_1 + M) \cdot j\omega(L_2 + M) \\ (1 + hfe) + j\omega(L_1 + M) \cdot \frac{1}{j\omega c} = 0$$

$$\Rightarrow hie \cdot j\omega \left( L_1 + L_2 + 2M + \frac{1}{j^2 \omega^2 c} \right) + j^2 \omega^2 (L_1 + M)(L_2 + M) \\ (1 + hfe) + \frac{(L_1 + M)}{c} = 0$$

$$\Rightarrow hie \cdot j\omega \left[ (L_1 + L_2 + 2M) - \frac{1}{\omega^2 c} \right] - \omega^2 (L_1 + M)(L_2 + M) \\ (1 + hfe) + \frac{(L_1 + M)}{c} = 0$$

Now,

$$-\omega^2 (L_1 + M)(L_2 + M)(1 + hfe) + \frac{(L_1 + M)}{c} = 0$$

$$\Rightarrow -\omega^2 (L_1 + M)(L_2 + M)(1 + hfe) = \frac{-L_1 - M}{c}$$

$$\Rightarrow \cancel{\frac{\omega^2}{\omega^2}} = \frac{(L_1 + M)/c}{(L_1 + M)(L_2 + M)} = (1 + hfe)$$

$$\Rightarrow (1 + hfe) = \frac{1}{\omega^2 c (L_2 + M)}$$

$$\omega^2 = \frac{1}{(L_1 + L_2 + 2M)c}$$

keeping the value of  $\omega^2$ ,

$$1 + h_{fe} = \frac{(L_1 + L_2 + 2M)c}{c(L_2 + M)}$$

$$h_{fe} = \frac{L_1 + L_2 + 2M}{L_2 + M}$$

$$= \frac{L_1 + L_2 + 2M - L_2 - M}{L_2 + M}$$

$$\therefore h_{fe} = \frac{L_1 + M}{L_2 + M}$$

Ques. Again,

$$\text{h.e. } j\omega (L_1 + L_2 + 2M - \frac{1}{\omega^2 c}) = 0$$

$$\Rightarrow L_1 + L_2 + 2M - \frac{1}{\omega^2 c} = 0$$

$$\Rightarrow \frac{1}{\omega^2 c} = L_1 + L_2 + 2M$$

$$\Rightarrow \omega^2 = \frac{1}{c(L_1 + L_2 + 2M)}$$

$$\therefore \omega = \frac{1}{\sqrt{c(L_1 + L_2 + 2M)}}$$

$$\therefore f = \frac{1}{2\pi\sqrt{c(L_1 + L_2 + 2M)}}$$

Q9

→ What is hybrid parameters?

The constant  $h_{11}$ ,  $h_{12}$ ,  $h_{21}$  and  $h_{22}$  are called the hybrid (or h) parameters of the two port network.  $h_{11}$  has the dimension of impedance,  $h_{12}$  and  $h_{21}$  are dimensionless and  $h_{22}$  has the dimension of admittance. Thus, these ~~parameters~~ parameters are dimensionally homogeneous. That is why these parameters are called hybrid parameters. These parameters are most suitable for transistor testing.

## RC phase shift oscillator:

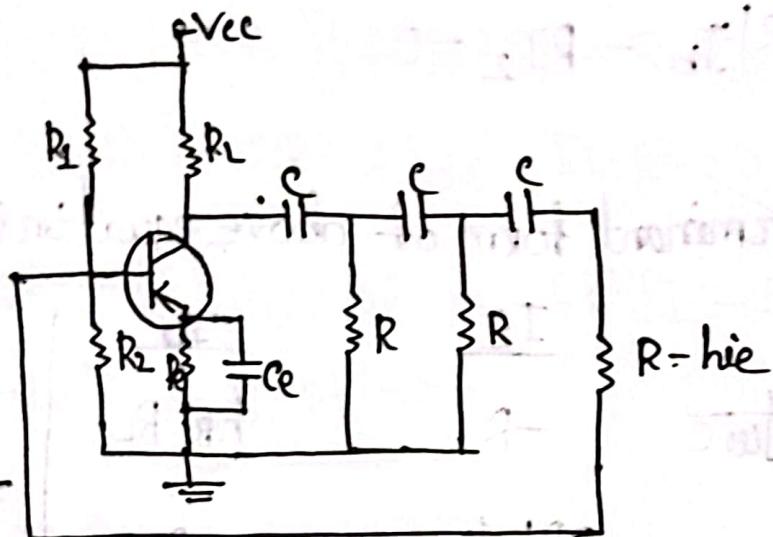


Fig: Phase shifter oscillator.

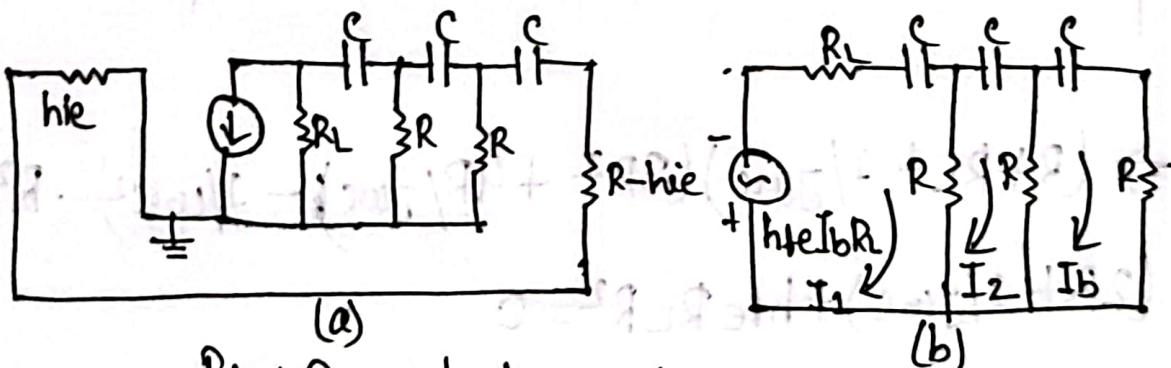


Fig: Equivalent circuit for phase shifter.

Applying KVL for three loops in fig-b:

For 1st loop:

$$(R + R_L + \frac{1}{j\omega C})I_1 - RI_2 + h_{fe} R_L I_b = 0$$

For second loop:

$$(\frac{1}{j\omega C} + 2R)I_e - RI_b - RI_1 = 0$$

51

for third loop,

$$\left(\frac{1}{j\omega c} + 2R\right)I_b - RI_2 = 0$$

The determinant form of above equation is given by:

$$\begin{vmatrix} I_1 & I_2 & I_b \\ R + RL + \frac{1}{j\omega c} & -R & hfe \cdot RL \\ -R & 2R + \frac{1}{j\omega c} & -R \\ 0 & -R & 2R + \frac{1}{j\omega c} \end{vmatrix} = 0$$

$$\Rightarrow (R + RL + \frac{1}{j\omega c})(3R^2 + 4R/\omega c) - \frac{1}{(\omega c)^2} - R^2$$

$$(2R + \frac{1}{j\omega c}) + hfe \cdot RL \cdot R^2 = 0$$

$$\Rightarrow (R + RL)(3R^2 - \frac{1}{(\omega c)^2}) - (R + RL)(j4R/\omega c) - j(3R^2/\omega c - \frac{1}{(\omega c)^3}) - 4R/\omega c^2 - 2R^3 + (jR^2/\omega c) + hfe \cdot RL \cdot R^2 = 0$$

Equating the imaginary part to zero, we get,

$$-(R + RL)(4R/\omega c) - \{(3R^2/\omega c) - (1/\omega c^3)\} + RL/\omega c = 0$$

$$\Rightarrow 3R^3 - R/\omega_2 c^2 + 3R^2 R_L - R_L/\omega_2 c^2 - 4R/\omega_2 c^2 - 2R^3 + h_{fe} R_L R^2 = 0$$

$$\Rightarrow 3R^3 - R\{GR^2 + 4R \cdot R_L\} + 3R^2 R_L - R_L\{GR^2 + 4R \cdot R_L\} - 4R\{GR^2 + 4R \cdot R_L\} - 2R^3 + h_{fe} \cdot R_L \cdot R^2 = 0$$

$$\Rightarrow 3R^3 - 6R^3 - 4R^2 \cdot R_L + 3R^2 R_L - 6R^2 R_L - 4R R_L^2 - 24R^3 - 16R^2 R_L - 2R^3 + h_{fe} R_L \cdot R^2 = 0$$

$$h_{fe} = 29 \frac{R}{R_L} + 23 + 4 \frac{R_L}{R}$$

$$= 23 + 29 \frac{R}{R_L} + 4 \frac{R_L}{R}$$


$$\omega^2 = \frac{1}{c^2 (6R^2 + 4R \cdot R_L)}$$

$$\therefore \omega = \frac{1}{c \sqrt{(6R^2 + 4R \cdot R_L)}}$$

$$\therefore f = \frac{1}{2\pi c} \cdot \frac{1}{\sqrt{(6R^2 + 4R \cdot R_L)}}$$

53

## Wien bridge oscillator:

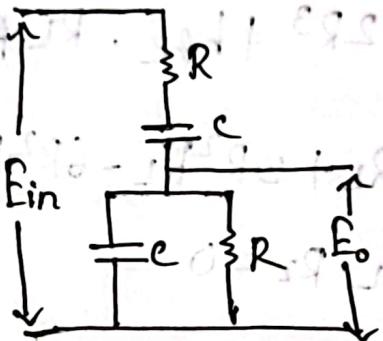

$$\text{for series circuit, } = R + \frac{1}{j\omega C}$$

$$= R + \frac{j\omega}{j^2\omega C}$$

$$= R - \frac{j}{\omega C}$$

for parallel circuit,

$$= -\frac{R \cdot j}{\omega C}$$

$$= \frac{-R \cdot j}{R - j/\omega C} = E_o$$

$$\therefore \text{Total impedance} = R - \frac{j}{\omega C} - \frac{Rj/\omega C}{R - j/\omega C}$$

$$\therefore \frac{E_o}{E_{in}} = \frac{\text{Impedance in parallel combination}}{\text{Total impedance}}$$

$$= \frac{-R\ddot{J}/we}{R - \frac{\ddot{J}}{we} - \frac{R\ddot{J}/we}{R - \frac{\ddot{J}}{we}}}$$

$$\frac{-R\ddot{J}/we}{R - \frac{\ddot{J}}{we}}$$

$$= \frac{R - \frac{\ddot{J}}{we} - \frac{R\ddot{J}/we}{R - \frac{\ddot{J}}{we}}}{R - \frac{\ddot{J}}{we}}$$

$$= \frac{-R\ddot{J}/we}{R - \frac{\ddot{J}}{we}} \times \frac{1}{R - \frac{\ddot{J}}{we} - \frac{R\ddot{J}/we}{R - \frac{\ddot{J}}{we}}}$$

$$= \frac{-R\ddot{J}/we}{(R - \frac{\ddot{J}}{we})^2 - (R - \frac{\ddot{J}}{we}) \left( \frac{R\ddot{J}/we}{R - \frac{\ddot{J}}{we}} \right)}$$

$$= \frac{-R\ddot{J}/we}{(R - \frac{\ddot{J}}{we})^2 - \frac{\ddot{J}R}{we}}$$

$$= \frac{-R\ddot{J}/we}{R^2 - 2.R.\frac{\ddot{J}}{we} + \frac{\ddot{J}^2}{we^2 c^2} - \frac{\ddot{J}R}{we}}$$

$$= \frac{-R\ddot{J}/we}{R^2 + \frac{\ddot{J}^2}{we^2 c^2} - \frac{3R\ddot{J}}{we}}$$

55

There is zero phase shift if the term in  $\boxed{J}$  vanishes.

$$R^2 + \frac{J}{\omega^2 C^2} = R^2 - \frac{1}{\omega^2 C^2}$$

$$\Rightarrow R^2 - \frac{1}{\omega^2 C^2} = 0$$

$$\Rightarrow R^2 = \frac{1}{\omega^2 C^2}$$


$$\Rightarrow \rho \omega^2 = \frac{1}{R^2 C^2}$$

$$\therefore \omega = \frac{1}{RC}$$

$\therefore$  frequency of oscillation in Wien bridge

$$f = \frac{1}{2\pi RC}$$

### Crystal oscillator:

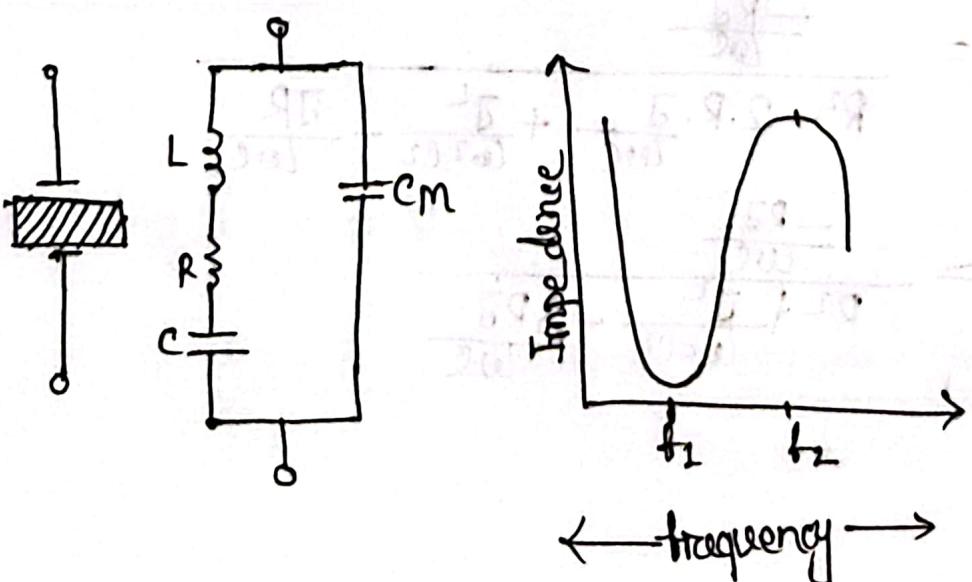

The impedance vs frequency curve is shown in fig. It is obvious from the figure that there exists one resonant condition when the reactances of the series RLC leg are equal and opposite. At this condition, the series-resonant impedance is very low. Thus at series-resonance:

$$\omega_s L - \frac{1}{\omega_s C} = 0$$

$$\Rightarrow \frac{\omega_s^2 L C - 1}{\omega_s C} = 0$$

$$\Rightarrow \omega_s^2 L C - 1 = 0$$

$$\Rightarrow \omega_s^2 L C = 1$$

$$\Rightarrow \omega_s^2 = \frac{1}{L C}$$

$$\therefore \omega_s = \frac{1}{\sqrt{L C}}$$

$$\therefore f_s = \frac{1}{2\pi\sqrt{L C}}$$

The other resonant occurs at a higher frequency when the reactance of the series resonant leg equals the reactance of capacitor  $C_m$ . This is parallel resonance and or antiresonance condition of the crystal. At the frequency the crystal offers a very

57

high impedance to the external circuit. In this case:

$$\omega_p L - \frac{1}{\omega_p C} = \frac{1}{C_p C_m}$$

$$\Rightarrow \omega_p L = \frac{1}{C_p C_m} + \frac{1}{\omega_p C}$$

$$\Rightarrow \omega_p L = \frac{C + C_m}{C_p C_m}$$

$$\Rightarrow \omega_p \cdot \omega_p = \frac{C + C_m}{L \cdot C \cdot C_m}$$

$$\Rightarrow \omega_p^2 = \frac{C + C_m}{L \cdot C \cdot C_m}$$

$$\therefore \omega_p = \sqrt{\frac{C + C_m}{L \cdot C \cdot C_m}}$$

$$\therefore f_p = \frac{1}{2\pi} \sqrt{\frac{C + C_m}{L \cdot C \cdot C_m}}$$

### Colpitt's Oscillator:

General equation of oscillator:

$$hie(z_1 + z_2 + z_3) + z_1 z_2 (1 + h_{fe}) + z_1 z_3 = 0 \quad \text{--- (1)}$$

In case of Colpitt's oscillator,

$$\begin{aligned} z_1 &= \frac{1}{j\omega C_1}, \quad z_2 = \frac{1}{j\omega C_2}, \quad z_3 = j\omega L \\ &= -\frac{j}{\omega C_1} \quad \quad \quad = -\frac{j}{\omega C_2} \end{aligned}$$

Substituting the values in equation (1),

$$\begin{aligned} &hie \left( -\frac{j}{\omega C_1} - \frac{j}{\omega C_2} + j\omega L \right) + \left( -\frac{j}{\omega C_1} \right) \left( -\frac{j}{\omega C_2} \right) (1 + h_{fe}) + \left( -\frac{j}{\omega C_1} \right) j\omega L = 0 \\ \Rightarrow &-jhie \left( \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right) + \frac{j^2 (1 + h_{fe})}{\omega^2 C_1 C_2} - \frac{j^2 L}{C_1} = 0 \\ \Rightarrow &-jhie \left( \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right) - \frac{(1 + h_{fe})}{\omega^2 C_1 C_2} + \frac{L}{C_1} = 0 \quad [j^2 = -1] \end{aligned}$$

The frequency of oscillation can be obtained by equating the imaginary part to zero:

$$-jhie \left( \frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right) = 0$$

$$\Rightarrow \frac{C_2 + C_1 - \omega^2 C_1 C_2 L}{\omega^2 C_1 C_2} = 0$$

59

$$\Rightarrow C_2 + C_1 - \omega^2 C_1 \cdot C_2 \cdot L = 0$$

Unbilled circuit

$$\Rightarrow \omega^2 = \frac{C_2 + C_1}{C_1 \cdot C_2 \cdot L}$$

$$\Rightarrow \omega = \sqrt{\frac{(C_2 + C_1)}{C_1 \cdot C_2 \cdot L}}$$

$$\therefore f = \frac{1}{2\pi} \sqrt{\frac{(C_2 + C_1)}{C_1 \cdot C_2 \cdot L}}$$

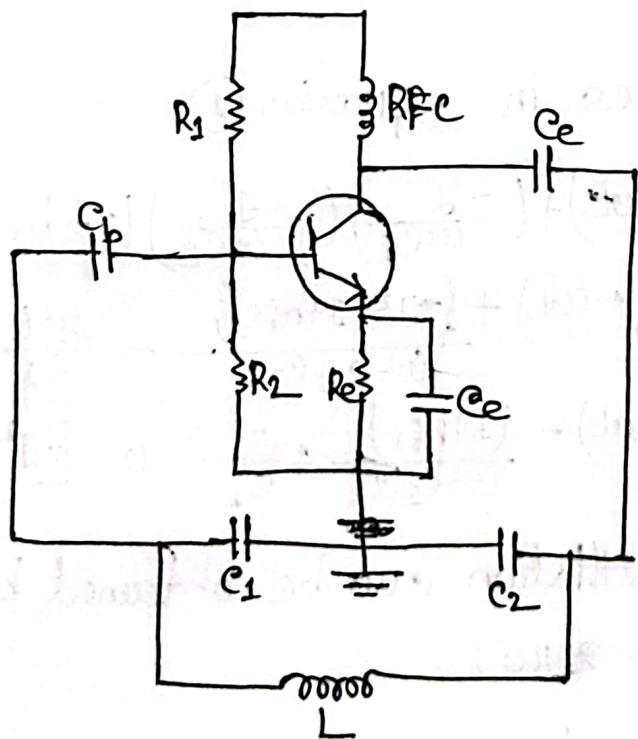


Fig : Colpitt's Oscillator

## Filter Circuit

filter: filters are electrical networks used to separate alternating from direct current components or to separate a group of a.c. components included within a particular frequency from those lying outside this range.

There are two types of filters:



- ① Active filter
- ② Passive filter

Frequency response এর ক্ষেত্র নিচে দেখো:

- ① Low pass filter
- ② High pass filter
- ③ Band pass filter
- ④ Band stop filter.

61

## Band pass filter:

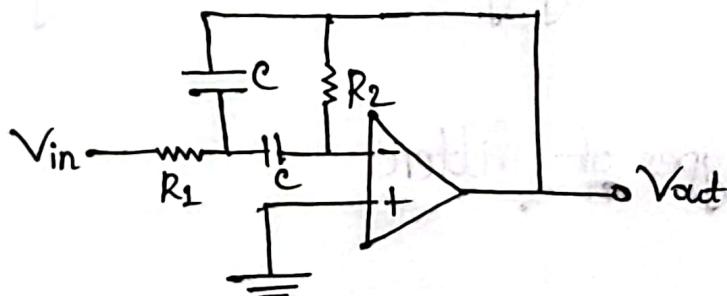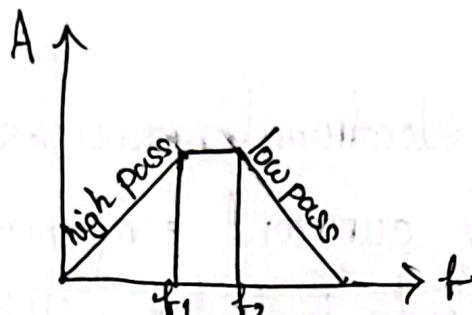

$$\text{Gain } Av = \frac{-R_2}{2R_1}$$

$$f_o = \frac{1}{\sqrt{f_1 f_2}}$$


$$f_o = \frac{1}{2\pi e \sqrt{R_1 R_2}}$$

$$\Omega = \frac{f_o}{BW} = \frac{1}{2} \sqrt{\frac{R_2}{R_1}} \quad [BW = \text{Bandwidth}]$$

If,  $\Omega > 1$  [Narrow band filter]

$\Omega < 1$  [wide band filter]

## Band stop filters:

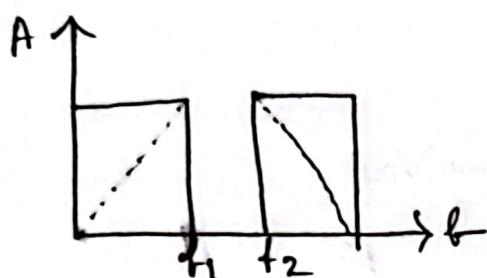


frequency response of band pass filter.



63

### Low pass filter (Integrator):

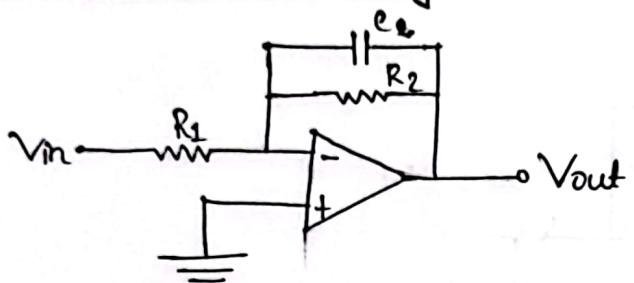


Voltage gain  $A_v = -\frac{R_2}{R_1}$


$$f_c = \frac{1}{2\pi R_2 C}$$

$$X_C = \frac{1}{2\pi f_c}$$

### frequency response:

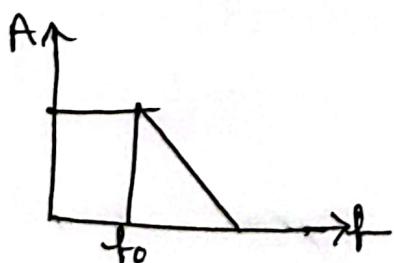


## High-pass filter (Differentiator):

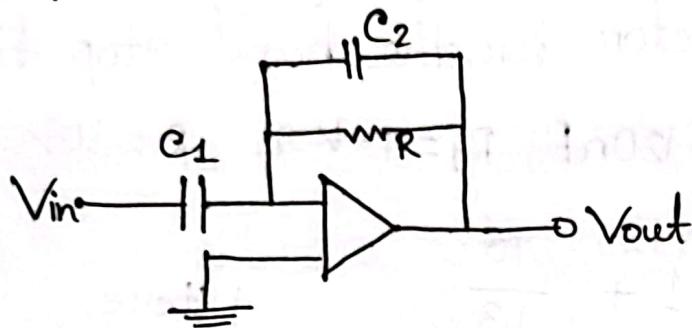

$$\begin{aligned}\text{Voltage gain} &= -\frac{X_C_2}{X_C_1} \\ &= -\frac{R_f}{R_1}\end{aligned}$$

Frequency response:

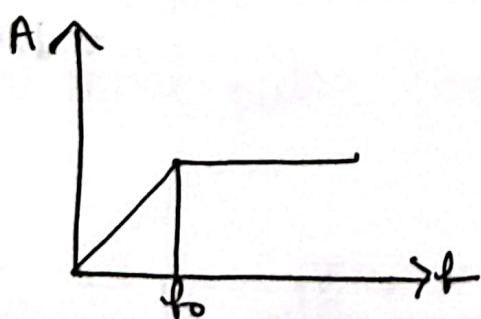

→ Operation Exam 9

65

\*\*\*

Question: What are the voltage gain, centre frequency and Q factor for the band stop filter if,  $R = 22\text{ k}\Omega$ ,  $C = 120\text{ nF}$ ,  $R_1 = 13\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$

$$A_v = 1 + \frac{R_2}{R_1} = 1 + \frac{10}{13} \\ = 1.77$$

Centre frequency,

$$f_0 = \frac{1}{2\pi RC} \\ = \frac{1}{2\pi \times 22 \times 10^3 \times 120 \times 10^{-9}} \\ = 60.3 \text{ Hz}$$

Here,

$$R_1 = 13 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$A_v = ?$$

$$f_0 = ?$$

$$R = 22 \text{ k}\Omega$$

$$= 22 \times 10^3 \text{ }\Omega$$

$$C = 120 \text{ nF}$$

$$= 120 \times 10^{-9} \text{ F}$$

and,

$$\phi = \frac{0.5}{2 - A_v} \\ = \frac{0.5}{2 - 1.77} \\ = 2.17$$

## Multivibrator

Definition: A multivibrator is a two-stage resistance coupled amplifier with positive feedback from the output of one amplifier to the input of the other. It has two state : ON and off.


Multivibrators are classified into three types :

1. Astable multivibrator: An astable multivibrator is such a circuit that it automatically switches between the two states continuously without the application of any external pulse for its operation.

2. Monostable multivibrator: A monostable multivibrator has a stable state and a quasi-stable state. This has a trigger input to one transistor. So, one transistor changes its state automatically, while the other one needs a trigger input to change its state.

As this multivibrator produces a single output for each trigger pulse, this is known as One-shot multivibrator. This multivibrator can not stay in quasi-stable state for a longer period while it stays in stable state until trigger pulse is received.

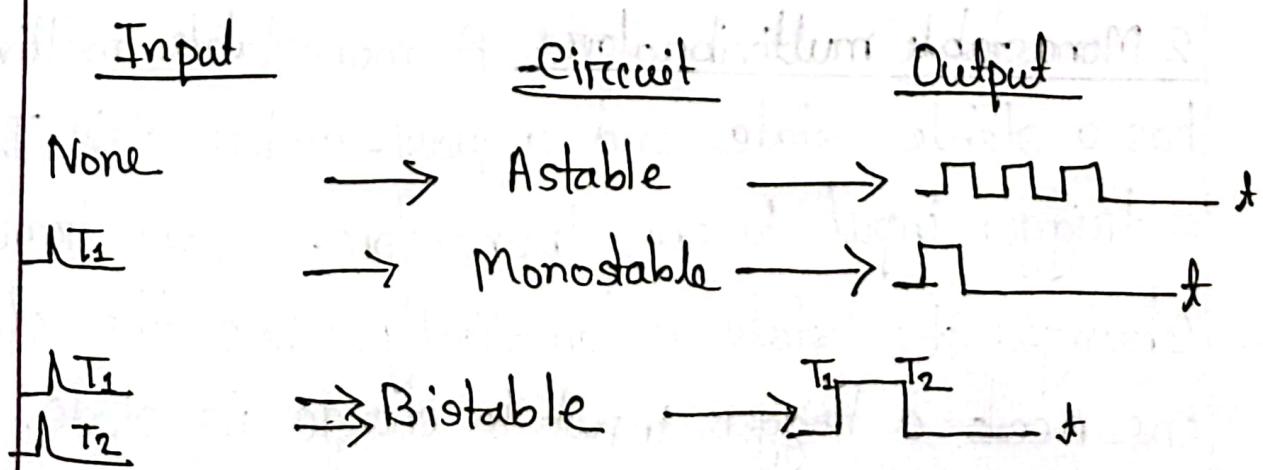3. Bistable multivibrator: A bistable multivibrator has both the two states stable. It requires two trigger pulses to be applied to change the states. Until the trigger input is given, this multivibrator cannot change its state. It's also known as flip-flop multivibrator.



Trigger: ON/OFF করায় এন্ড বাঁধে থেকে এই signal দ্বারা নির্দিষ্ট